



# Power Electronics

08.09.2014

<b>Surname:</b>					<b>Student number:</b>																										
<table border="1" style="width: 100%; height: 20px;"> <tr> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> </tr> </table>																				<table border="1" style="width: 100%; height: 20px;"> <tr> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> </tr> </table>											
<b>First name:</b>																															
<table border="1" style="width: 100%; height: 20px;"> <tr> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> </tr> </table>																															
<b>Course of study:</b>																															
Task:	1	2	3	4		Total		Mark																							
(Points)	(25)	(25)	(25)	(25)		(100)																									

**Duration: 120 minutes**

**Permitted resources:**

- a non-programmable calculator without graphic display
- drawing materials (compasses, protractor, ruler, pens ...)


**Please note:**

- Please prepare your student ID card (with photo) on your desk for the attendance check.
- Please label each exam sheet with your name and student number. Use a new exam sheet for each task. Do not use pencils or red pens.
- With numerical calculations, the units must be considered in every step. Not following that rule will result in deduction of points.
- All solutions must be clearly documented and wherever required explained! The entry of a mere final result without any approach will not be counted.

## Good Luck!

**Task 1: Boost Converter****(25 Points)**

Figure 1 shows a boost converter. The input voltage to the converter is  $U_1 = 8\text{ V}$ . The average output voltage  $\bar{u}_2$  should be  $32\text{ V}$  while delivering a load with a DC content of  $4\text{ A}$ . The power-switches are assumed to be ideal during conduction and blocking states ( $0\text{ V}$  during conduction and  $0\text{ A}$  in blocking). The converter is operated at a switching frequency of  $25\text{ kHz}$ . The equivalent series resistance of the capacitor is given as  $R_C = 25\text{ m}\Omega$  and the capacitance as  $C = 500\text{ }\mu\text{F}$ .

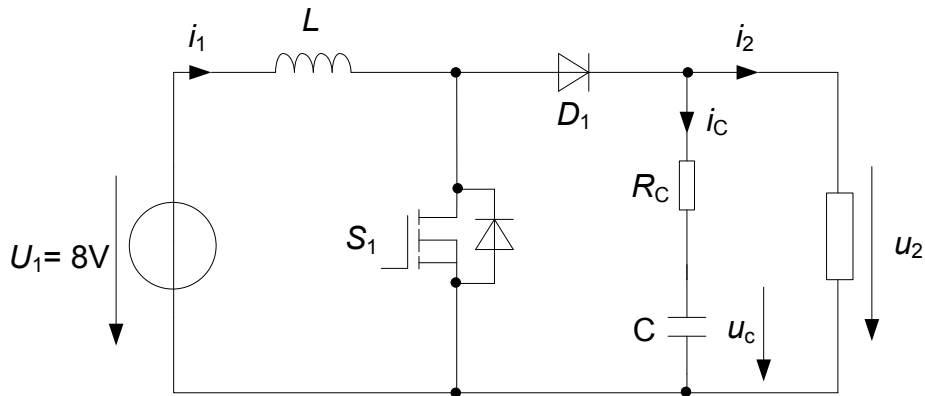**Figure 1: Boost converter**


Note: For questions 1.1 to 1.5,  $R_C$  can be considered zero.

Estimate the following:

- 1.1 The DC content of the input current  $i_1$ .
- 1.2 Evaluate the inductance  $L$  to limit the ripple current of  $i_1$  to 20% of the DC content (assume the output voltage approximately constant).
- 1.3 For what value of the inductance  $L$  does the converter operate at the boundary between continuous and discontinuous conduction modes?
- 1.4 Sketch the current through the capacitor  $C$  (assume the load current approximately constant)
- 1.5 Sketch  $u_C$ .
- 1.6 Assume that the above results remain valid even for a small value of  $R_C = 25\text{ m}\Omega$ . Evaluate the ripple voltage across  $R_C$ .

**Task 2: Buck converter****(25 Points)**


Figure 2 shows a non-ideal buck converter. The source and inductor resistances are represented by  $R_1$  and  $R_L$  respectively. The devices  $S_1$  and  $D_1$  are assumed to be ideal. The state variables are the inductor current  $i_L$  and capacitor voltage  $u_2$ . The circuit is to be operated in continuous conduction mode.

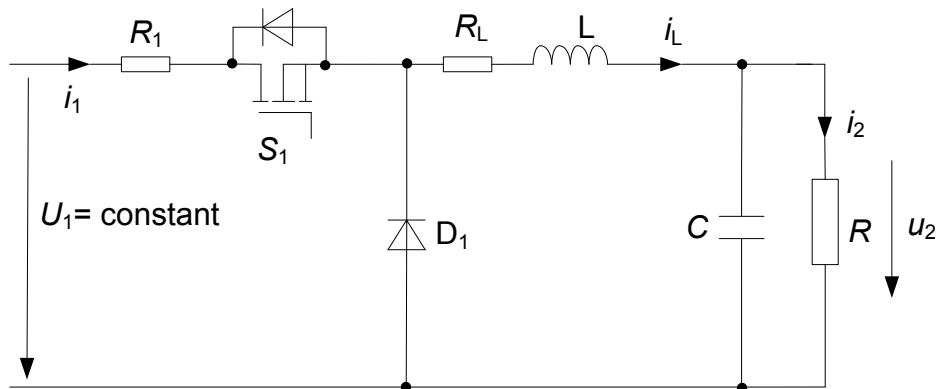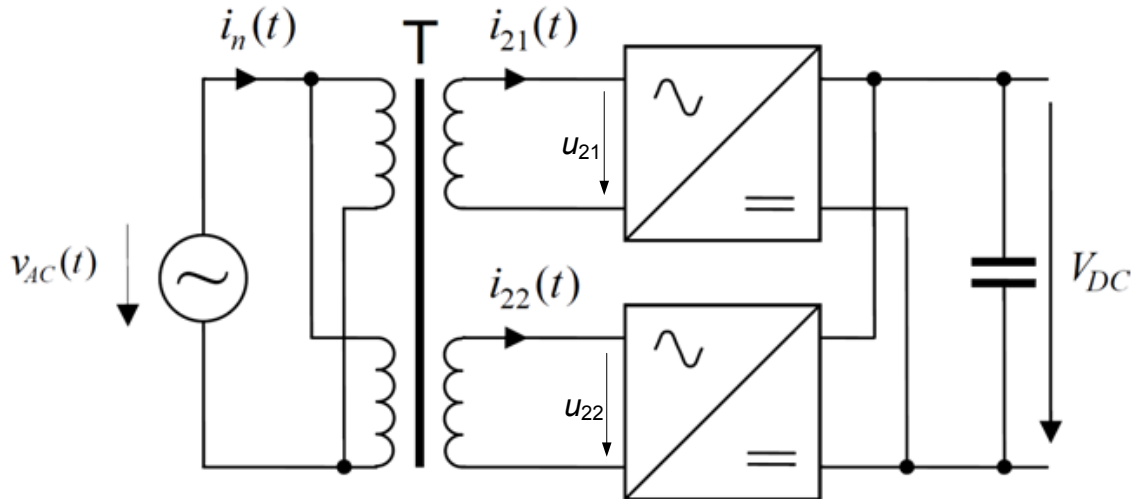**Figure 2: Buck converter**

- 2.1 Write down the differential equations of the converter for the two state variables during ON state i.e. when  $S_1$  is ON.
- 2.2 Write down the differential equations of the converter for the two state variables during OFF state i.e. when  $S_1$  is OFF.
- 2.3 Using the above write down the averaged dynamic model of the converter in state space matrix notation.
- 2.4 Derive the gain  $\bar{u}_2/U_1$  at steady state as a function of the duty cycle.
- 2.5 Evaluate the efficiency of the converter based on the average modeling  $\eta = (\bar{u}_2 \bar{i}_2)/(U_1 \bar{i}_1)$

**Task 3: Four-Quadrant Converter****(25 Points)**

A four-quadrant converter (4QC) is connected to the single-phase grid. The overhead line delivers a single-phase sinusoidal AC voltage  $V_{AC}$  with grid frequency  $f$ . The two four-quadrant converters are operated in interleaving operation to minimize the current ripple. The traction transformer has two primary windings connected in parallel and two secondary windings.

**Figure 3: Power supply for an electric locomotive**


Nominal output voltage	$V_{DC} = 1.8 \text{ kV}$	Grid voltage	$V_{AC} = 25 \text{ kV}$
Nominal output power	$P_N = 2.4 \text{ MW}$	Grid frequency	$f = 50 \text{ Hz}$
Transformer's nominal apparent power	$S_N = 2.6 \text{ MVA}$	Switching frequency	$f_S = 500 \text{ Hz}$
Transformer's short circuit voltage	$u_k = 19\%$		

(each secondary)

- 3.1** Draw the circuit diagram of a four-quadrant converter with the semiconductors treated as ideal switches.
- 3.2** Draw qualitatively the switching functions of the 4QC-switches of the two parallel four-quadrant converters in interleaving operation. Draw the transformer secondary voltages resulting from the two four-quadrant converters for a fundamental period.
- 3.3** Calculate the leakage inductances of the transformer. Assume that the primary leakage inductances can be neglected.
- 3.4** The two four-quadrant converters should be controlled that way that only active power is supplied from the grid (target power factor mode). Determine the phase angle of the required fundamental phasors of  $u_{21}$ ,  $u_{22}$ . Consider the case of nominal load at nominal input voltage.
- 3.5** Calculate the minimum required transformer winding ratio  $\alpha = \frac{N_1}{N_2}$  for the case of 3.4.
- 3.6** Calculate the peak voltage stress in the transistors and the diodes of the 4QC. Explain in words what has to be done to calculate the peak current stress (calculation not mandatory).

**Task 4: Line-Commutated Converter****(25 Points)**

A line-commutated converter in M2-configuration supplies a DC-motor with a well smoothed armature current shown in figure below.

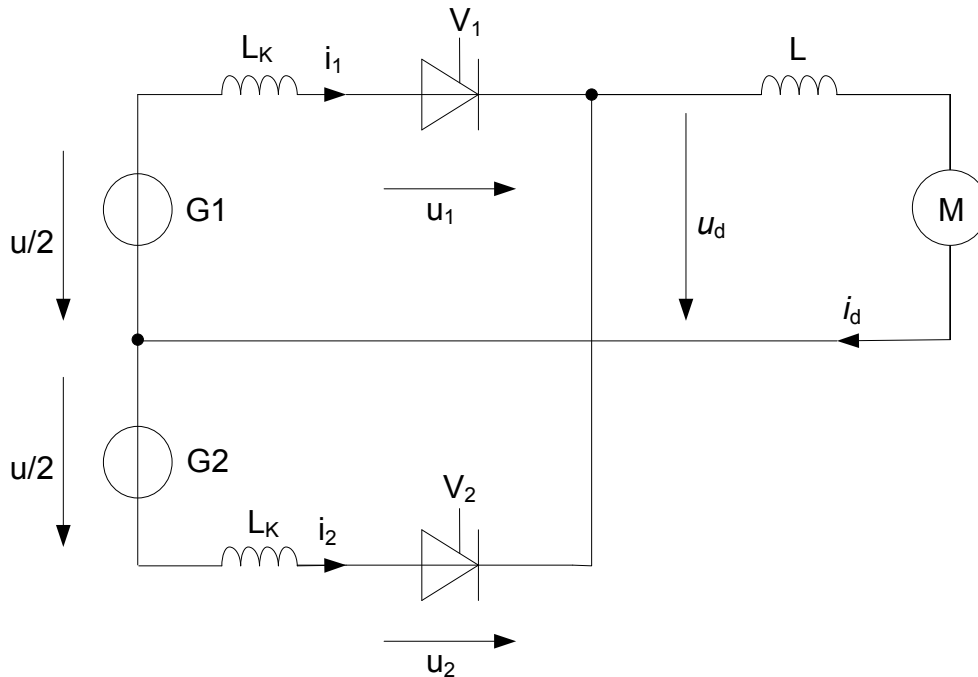

**Figure 4: Line-commutated converter in M2-configuration**

- 4.1** Sketch qualitatively the resulting waveforms for thyristor currents  $i_1$ ,  $i_2$ , the thyristor voltages  $u_{T1}$ ,  $u_{T2}$  and the output voltage  $u_d$  for a control angle of  $\alpha = 45^\circ$  assuming ideal commutations.
- 4.2** Derive a formula for the current  $i_1$  during commutation for  $\alpha = 0$ .
- 4.3** Calculate the inductive voltage drop due to the commutation.
- 4.4** Calculate the maximum control angle  $\alpha_{max}$  if the commutating inductors are  $L_K = 1 \text{ mH}$ , the output current is  $I_d = 50 \text{ A}$ , the recovery time of the thyristors to block the recurring positive voltage is  $t_c = 300 \mu\text{s}$  and the line voltage amplitude is  $400 \text{ V}$ .

