

Exercise 10: 6-Pulse Bridge Circuit

For the assembly of a converter supplied DC drive train the following devices will be used:

Three-phase transformer:

Rated power:	$S_{Tr} = 180 \text{ kVA}$	Equivalent resistance per phase:	$R = 8 \text{ m}\Omega$
Nominal secondary line voltage:	$U_{LN} = 400 \text{ V}$	Equivalent inductance per phase:	$L = 0.1 \text{ mH}$

DC motor:

Nominal power:	$P_N = 160 \text{ kW}$	Resistance of armature circuit:	$R_A = 25 \text{ m}\Omega$
Nominal voltage:	$U_{AN} = 440 \text{ V}$	Inductance of armature circuit:	$L_A = 2 \text{ mH}$
Nominal current:	$I_{AN} = 390 \text{ A}$		

Smoothing inductor:

Inductance:	$L_{Dr} = 4 \text{ mH}$	Resistance:	$R_{Dr} = 5 \text{ m}\Omega$
-------------	-------------------------	-------------	------------------------------

Thyristors:

Threshold voltage:	$U_{T0} = 1 \text{ V}$	Equivalent resistance:	$r_T = 1.5 \text{ m}\Omega$
Recovery time:	$t_q = 200 \text{ }\mu\text{s}$		

- Which converter topology is suitable for this application and why?
- Draw the equivalent circuit diagram for this arrangement and write the formula to calculate $U_{d\alpha}$. Determine the firing angle α_N for nominal operation.
- Which control angle α_3 has to be set if the line voltage has dropped by 5% and the DC motor shall still be supplied with nominal voltage and current? How many percent P_U does the maximum available converter voltage U_{di0} lie above the required voltage?
- Determine the maximal stress of the thyristors at nominal operation in case of ideal smoothed motor current with regard to
 - periodic peak blocking voltage U_{TRR} .
 - the arithmetic average current $I_{T(AV)}$ and the root mean square current $I_{T(RMS)}$.
 - power losses P_T .
 - the current slope di/dt .
- Calculate the efficiency η_A of the complete drive train (neglect the excitation losses) and the efficiency η_{SR} of the converter at nominal operation.
- For the analysis of the commutation, I_d and L_k are assumed to be constant. Draw the equivalent circuit diagram of the commutation loop when V_3 (phase 3) commutates to V_1 (phase 1). Calculate the overlap time at nominal operation. The commutation resistances (R_k) can be neglected.

7. Use the results from problem 6 and the auxiliary sheet below to draw the waveform of the output voltage and the voltage at the switch V_1 . Draw the overlap time and the protection time as well.
8. Determine the maximum control angle α for the worst case condition if the protection time is twice as high as the recovery time at $U_{LN} = 400\text{ V} \pm 10\%$.

Auxiliary diagram for problem 7

