

1 Buck Converter with RCD Snubber

Figure 1 shows the circuit diagram of a Buck-Converter which is used to supply the D.C. clutch drive of an electrical fork lifter. The output current is additionally smoothed by the ripple filter choke L_G .

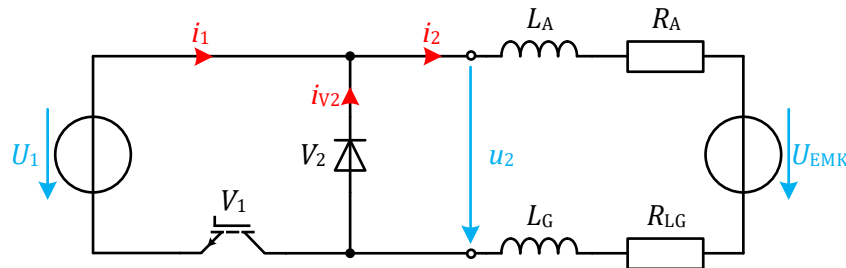


Figure 1: Buck-Converter

The following values are known:

- Input voltage: $U_1 = 120 \text{ V}$
 - Induced counter voltage: $U_{EMK} = 60 \text{ V}$
 - Armature inductance: $L_A = 500 \mu\text{H}$
 - Ripple filter choke: $L_G = 1.5 \text{ mH}$
 - Load resistance ($R_L = R_A + R_{LG}$): $R_L = 0.5 \Omega$
 - Switching period: $T_S = 0.5 \text{ ms}$
 - Time constant of the ohmic-inductive load: $\tau_L = (L_A + L_G)/R_L$
1. Calculate the turn-on-time T_e when the output current becomes discontinuous ($i_2(0) = i_2(T_S)$) and sketch the temporal current and voltage waveforms of u_2, i_1, i_2 and i_{V2} . How much do the temporal waveforms change if the turn-on-time is reduced to the half of the calculated value?
 2. Sketch the proportion of U_{EMK}/U_1 for a variable T_e/T_S when the Buck-Converter operates in boundary conduction mode and
 - a) $\tau_L = 0.2 \cdot T_S$
 - b) with negligible R_L
 3. How much are the mean value of the output current I_2 and the ripple of the output current Δi_2 if the Buck-Converter operates in steady state with $T_e = 0.35 \text{ ms}$?

The RCD snubber circuit around the switching transistor V_1 prevents the invalid high voltages that appear due to the parasitic leakage inductances $L_{S1} \dots L_{S4}$ of the wiring and voltage source.

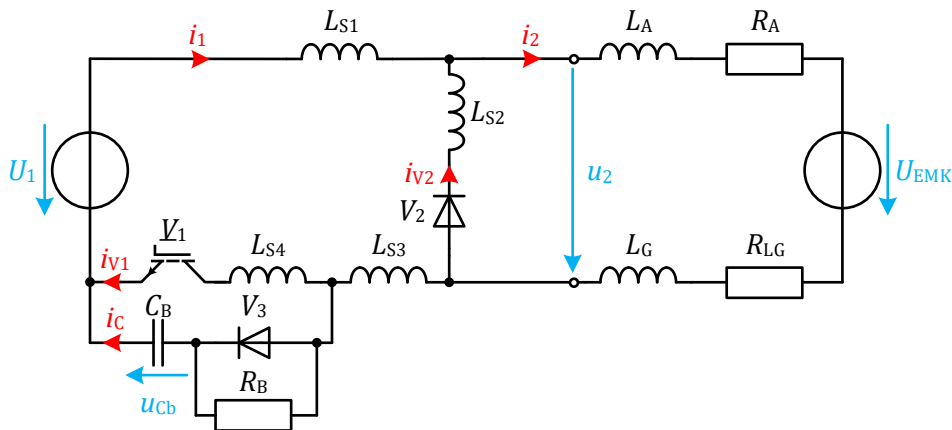


Figure 2: Buck-Converter with RCD-Snubber and leakage inductances

The following values are also known:

- Leakage inductances:
 - $L_{S1} = 2 \mu\text{H}$
 - $L_{S2} = L_{S3} = L_{S4} = 100 \text{ nH}$
4. Calculate the temporal voltage waveforms of the capacitor voltage u_{C_B} and the transistor voltage u_{C_E} right after the turn-off event and with the following assumptions:
 - a) The output current is constant during the turn-off process $I_2 = 50 \text{ A}$
 - b) The transistor current i_{V_1} decreases within the turn-off time $t_f = 1 \mu\text{s}$ until it reaches zero.
 - c) The RCD snubber circuit has ideal components.
 5. Compute the capacitance of C_B for the given specification of $u_{C_E} \leq 2 \cdot U_1$.
 6. Calculate the power loss P_V of the resistor R_B if the Buck-Converter operates in periodically switching mode. Determine the maximum valid value of the switching frequency for a specified loss of $P_V \leq 50 \text{ W}$ on the condition that the whole energy, stored in the capacitor C_B , is transformed to heat in the resistor R_B .