

# 1 Quasi-Resonant Buck Converter

By adding a resonant tank ( $L_r$ ,  $C_r$ ) within the switches  $V_1$  and  $V_2$ , a conventional Buck Converter is modified to a quasi-resonant Buck Converter.

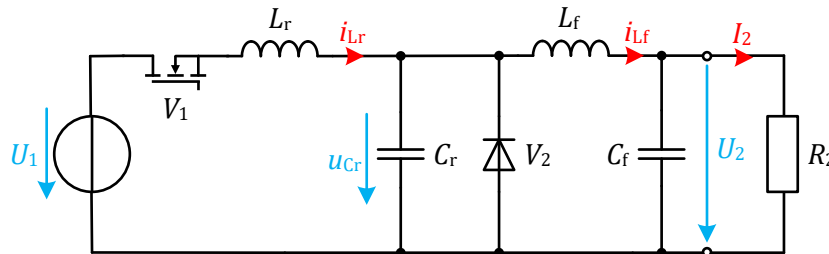


Figure 1: Buck Converter with resonant tank

The following values are known:

- Output current:  $I_2 = 10 \text{ A}$
- Input voltage:  $U_1 = 10 \text{ V}$
- Resonant choke:  $L_r = 320 \text{ nH}$
- Resonant capacitor:  $C_r = 500 \text{ nF}$
- Switching period:  $T_S = 0.5 \text{ } \mu\text{s}$

On the condition  $L_r \ll L_f$  and  $C_r \ll C_f$  the network  $L_f$ ,  $C_f$  and  $R_2$  can be replaced by a constant current source during the time of one switching period. The input voltage source and semi-conductors are considered as ideal.

1. The state, where free-wheeling diode  $V_2$  conducts the filter current  $i_{Lf} = I_2$ , is the initial point in order to investigate the course of events in one switching period. After the transistor  $V_1$  is switched on, the circuit passes through three different states before the initial point is reached. Again the transistor is switched off immediately after zero current occurs. Sketch the equivalent circuits for all four possible switching states.
2. Compute the wave-shape of the capacitor  $u_{Cr}$  voltage and the transistor current  $i_{Lr}$  in all intervals of a switching period  $T_S$  and the duration of the intervals.
3. Sketch the qualitative wave-shape of the capacitor voltage  $u_{Cr}$  and the transistor current  $i_{Lr}$  for one switching period  $T_S$ .
4. Determine the DC voltage ratio  $U_2/U_1$ .