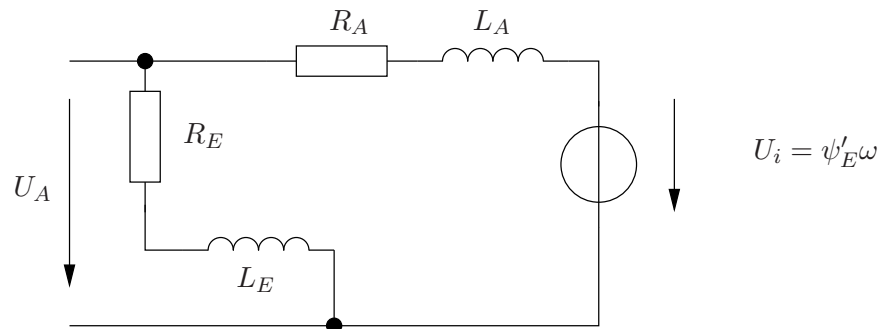


Exercise 8: DC shunt motor

A DC shunt motor (see figure) is given at the rated voltage $U_N = 220 \text{ V}$. The rated power is $P_N = 11 \text{ kW}$. With no-load, motor has the current $I = 5 \text{ A}$ at speed $n = 1150 \text{ min}^{-1}$. The armature resistance is $R_A = 0.5 \Omega$ and excitation resistance is $R_E = 110 \Omega$.



Questions:

a) At rated operation point

Calculate the following at rated operation point:

- the speed,
- the torque,
- and the efficiency,

of the motor.

b) Starting of motor

- Calculate the starting armature current of motor.
- Where must a series resistor be inserted.
- How much is the value of series resistor, if the starting armature current must be smaller than 150% of rated current.
- At what speed can it be bridged?